



**Faculty of Engineering & Technology**

**Electrical & Computer Engineering Department**

**COMPUTER ARCHITECTURE**

**ENCS4370**

**Course Project 2**

**Design and verify a simple RISC processor in Verilog**

---

**Prepared by:**

Rebal Zabade-1210162

Sondos Farrah-1200905

Mohammad Makhamreh -1200227

**Instructor:** Dr. Aziz Qaroush.

**Date:** 20<sup>th</sup> June 2024

**Section:** 3

## Abstract:

This project involves designing and verifying a multi-cycle RISC processor in Verilog. The 16-bit processor includes 8 general-purpose registers, a program counter, and supports R-type, I-type, J-type, and S-type instructions, encompassing 21 essential operations. The multi-cycle architecture executes instructions over multiple clock cycles, optimizing resource use and simplifying control logic. Verification includes creating a testbench and running code sequences to ensure functionality. The report details the Datapath, control path, control signal generation, and verification results, emphasizing correctness and completeness.

## Table of Contents

Abstract:.....	1
1. Theory: .....	4
1.1 Registers:.....	4
1.1.1 General-Purpose Registers:.....	4
1.1.2 Special-Purpose Register:.....	5
1.2 Multiplexer (MUX): .....	5
1.3 Instruction Memory:.....	6
1.4 Register File:.....	6
1.5 Sign-Extend Unit:.....	7
1.6 control unit: .....	7
1.7 Arithmetic Logic Unit (ALU): .....	8
1.8 Comparator:.....	8
1.9 Data Memory:.....	9
2- Procedure & Discussion: .....	10
2.1 Control Signals Table(Mohammad, Sondos, Rebal):.....	10
2.1.1 Details about signals(Rebal):.....	11
2.1.2 Expressions for Control Bits(Rebal):.....	12
2.1.3 Final Data path(Mohammad, Sondos, Rebal): .....	12
2.2 Modules:.....	13
2.2.1 Clock Generator (Mohammad): .....	13
2.2.2 Instruction Fetch (Sondos):.....	13
2.2.3 Data memory (Mohammad): .....	13
2.2.4 ALU(Rebal):.....	13
2.2.5 Control Unit (Rebal):.....	14
2.2.6 Comparator(Sondos):.....	14
2.2.7 PC (Mohammad): .....	14
2.2.8 Register file (Sondos):.....	14
2.2.9 Constants (Rebal):.....	15
2.2.9 CPU (Sondos, Mohammad):.....	15
3. Conclusion:.....	16
4. Appendices: .....	17
4.1 The code for Constants: .....	17
4.2 The code for comparator: .....	22
4.3 The code for Control Unit:.....	23
4.4 The code for alu:.....	32
4.5 The code for ClockGenerator:.....	34
4.6 The code for data Memory: .....	34
4.7 The code for instruction Memory: .....	36
4.8 The code for register File: .....	40
4.9 The code for riscProcessor:.....	41

## Table of Figure

Figure 1: General-Purpose Registers.....	4
Figure 2: Program Counter (PC) .....	5
Figure 3: MUX 2*1 .....	5
Figure 4: MUX 4*1 .....	5
Figure 5: Instruction Memory .....	6
Figure 6: Register File.....	6
Figure 7: Sign-Extend Unit .....	7
Figure 8: control unit.....	7
Figure 9: Arithmetic Logic Unit (ALU).....	8
Figure 10: Comparator .....	8
Figure 11: Data Memory .....	9
Figure 12: Final Data path.....	12
Figure 13: Clock Generator_tb.....	13
Figure 14: Instruction Fetch_tb .....	13
Figure 15: Data memory_tb .....	13
Figure 16: ALU_tb .....	13
Figure 17: Control Unit_tb.....	14
Figure 18: Comparator_tb .....	14
Figure 19: PC_tb .....	14
Figure 20: Register file_tb.....	14
Figure 21: Constants_code .....	15
Figure 22: CPU_tb .....	15

## Table of Table

Table 1: Control Signals.....	10
Table 2: Details about signals.....	11

## 1. Theory:

The design and verification of a multi-cycle RISC (Reduced Instruction Set Computing) processor involve several key theoretical concepts that form the foundation of modern computer architecture. This section outlines the essential theoretical aspects underpinning the project.

### 1.1 Registers:

#### Function:

- Store data, operands, and intermediate results for instructions.
- Provide fast access to frequently used data, minimizing access to slower main memory.


#### 1.1.1 General-Purpose Registers:

- **Number of Registers:** 8 (R0 to R7).
- **Size:** 16 bits each.
- **R0:** Hardwired to zero. Attempts to write to R0 are discarded.

#### Operations:

- **Read:** During the decode stage, source register values (e.g., Rs1 and Rs2) are read.
- **Write:** During the write-back stage, the result of an operation is written to the destination register (e.g., Rd).

General-Purpose Registers

 

*Figure 1: General-Purpose Registers*

### 1.1.2 Special-Purpose Register:

#### Program Counter (PC):

- **Function:** Holds the address of the next instruction to be fetched.
- **Operations:**
  - **Increment:** Increases by the instruction length (2 bytes for 16-bit instructions) after each fetch.
  - **Update:** Modified by jump and branch instructions to change the control flow.

 


Figure 2: Program Counter (PC)

### 1.2 Multiplexer (MUX):

Multiplexers are used to select between different data sources. In the data path, they route data based on control signals.

- **Function:** Directs the flow of data to different components based on control signals.
- **Operations:** Selects inputs for the ALU, register file, and other components.
- **Type:** 2\*1 MUX and 4\*1 MUX

 


Figure 3: MUX 2\*1

 
 


Figure 4: MUX 4\*1

### 1.3 Instruction Memory:

Instruction memory stores the program's instructions. It is read during the instruction fetch stage to retrieve the current instruction for execution.

- **Function:** Stores the machine code of the program.
- **Operations:** Read operation based on the address in the PC.

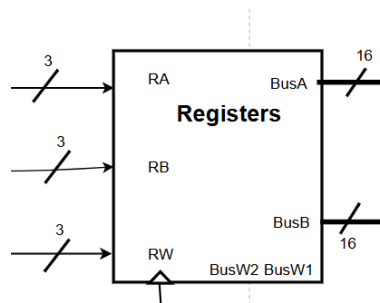


*Figure 5: Instruction Memory*

### 1.4 Register File:

The register file consists of multiple general-purpose registers. In this design, there are 8 registers (R0 to R7), with R0 hardwired to zero. It provides fast storage for temporary data and operands.

- **Function:** Stores intermediate data and operands for instructions.
- **Operations:** Read and write operations based on the instruction's register fields.



*Figure 6: Register File*

## 1.5 Sign-Extend Unit:

The extender unit is used to extend the bit-width of immediate values, ensuring they fit the processor's word size. It is crucial for handling signed and unsigned immediate values correctly.

- **Function:** Extends smaller bit-width immediate values to the full word size.
- **Operations:** Extends the sign of immediate values to ensure correct arithmetic operations.

 


Figure 7: Sign-Extend Unit

## 1.6 control unit:

The control unit generates control signals that orchestrate the operations of the datapath components. It ensures that each component performs the correct operation at the right time during the instruction execution cycle.

- **Function:** Controls the overall operation of the processor by generating appropriate control signals.
- **Operations:** Decodes the opcode and other fields to produce control signals for the Datapath.

 


Figure 8:control unit



## 1.7 Arithmetic Logic Unit (ALU):

The ALU performs arithmetic and logical operations. It is the computational core of the processor, executing operations specified by the instruction.

- **Function:** Performs arithmetic (e.g., addition, subtraction) and logical (e.g., AND, OR) operations.
- **Operations:** Takes inputs from registers or immediate values and produces a result.

 


Figure 9: Arithmetic Logic Unit (ALU)

## 1.8 Comparator:

The Comparator is responsible for comparing register values to determine the outcome of branch instructions. It helps decide the next address of the Program Counter (PC) based on specific conditions.

- **Function:** Compares two register values or a register value with zero to support conditional branch instructions.
- **Operations:**
  - Takes two inputs from the register file (BusA and BusB) or compares a register value with zero.
  - Produces a result of 1 or 0:
    - Result is **1** if the condition is met (branch taken).
    - Result is **0** if the condition is not met (branch not taken).


 


Figure 10: Comparator

## 1.9 Data Memory:

Data memory is used to store and retrieve data. It is accessed during load (LW, LBU, LBs) and store (Sv) instructions.

- **Function:** Provides storage for data to be loaded or stored during program execution.
- **Operations:** Read or write based on memory addresses calculated by the ALU.

 

*Figure 11: Data Memory*

## 2- Procedure & Discussion:

In this section, we will discuss the procedure followed to generate the control signals for each instruction type (R, I, S) in the multi-cycle RISC processor.

### 2.1 Control Signals Table(Mohammad, Sondos, Rebal):

The table below provides a detailed mapping of the input opcode to the output control signals for various instructions. This mapping ensures that the processor's Datapath correctly executes each instruction according to its type and specified operation.

Inst	Input	Output													
	op	PCSrc	RegSrc2	RegWr1	RegWr2	ALUSrc	ExtOp	ALUOP	AdressSig	DataInSig	MemRd	MemWr	Wbdata	modeSig	RegDst
AND	0000	0	0	1	0	0	0	1	x	x	0	0	0	x	0
ADD	0001	0	0	1	0	0	0	1	x	x	0	0	0	x	0
SUB	0010	0	0	1	0	0	0	1	x	x	0	0	0	x	0
ADDI	0011	0	x	1	0	1	0	1	x	x	0	0	0	x	0
ANDI	0100	0	x	1	0	1	0	1	x	x	0	0	0	x	0
LW	0101	0	x	1	0	1	0	1	0	x	1	0	1	x	0
Lbu	0110	0	x	1	0	1	1	1	0	x	1	0	1	x	0
LBs	0110	0	x	1	0	1	1	1	0	x	1	0	1	x	0
SW	0111	0	1	0	0	1	0	1	0	0	0	1	x	x	0
BGT_T	1000	2	1	0	0	x	1	x	x	x	0	0	x	0	0
BGT_NT	1000	0	1	0	0	x	1	x	x	x	0	0	x	0	0
BGTZ_T	1000	2	1	0	0	x	1	x	x	x	0	0	x	1	0
BGTZ_NT	1000	0	1	0	0	x	1	x	x	x	0	0	x	1	0
BLT_T	1001	2	1	0	0	x	1	x	x	x	0	0	x	0	0
BLT_NT	1001	0	1	0	0	x	1	x	x	x	0	0	x	0	0
BLTZ_T	1001	2	1	0	0	x	1	x	x	x	0	0	x	1	0
BLTZ_NT	1001	0	1	0	0	x	1	x	x	x	0	0	x	1	0
BEQ_T	1010	2	1	0	0	x	1	x	x	x	0	0	x	0	0
BEQ_NT	1010	0	1	0	0	x	1	x	x	x	0	0	x	0	0
BEQZ_T	1010	2	1	0	0	x	1	x	x	x	0	0	x	1	0
BEQZ_NT	1010	0	1	0	0	x	1	x	x	x	0	0	x	1	0
BNE_T	1011	2	1	0	0	x	1	x	x	x	0	0	x	0	0
BNE_NT	1011	0	1	0	0	x	1	x	x	x	0	0	x	0	0
BNEZ_T	1011	2	1	0	0	x	1	x	x	x	0	0	x	1	0
BNEZ_NT	1011	0	1	0	0	x	1	x	x	x	0	0	x	1	0
JMP	1100	1	x	0	0	x	x	x	x	x	0	0	x	x	0
CALL	1101	1	x	0	1	x	x	x	x	x	0	0	x	x	1
RET	1110	3	x	0	0	x	x	x	x	x	0	0	x	x	0
Sv	1111	0	x	x	0	x	0	x	1	1	0	1	x	x	0
		IF	ID	ID	ID	EX	ID	EX	MEM	MEM	MEM	MEM	WB	EX	ID

Table 1: Control Signals

### 2.1.1 Details about signals(Rebal):

Signal Name	Signal Description	Cases
PCSrc	Determines the next value of the PC	0: $PC = PC + 2$ 1: $PC = \{PC[15:10], \text{Immediate}\}$ 2: $PC = PC + \text{sign\_extended}(\text{Imm})$ 3: $PC = r7$
RegSrc2	Determines the second register	0: $RB = Rs2$ 1: $RB = Rd$
RegWr1	Determines the value to be written on the register	0: Indicates that no write operation should occur 1: write the value from stage 4 or 5
RegWr2	Write the value in the R7 in RF	0: Indicates that no write operation should occur 1: write the value if I have Call instruction
ALUSrc	Determines the first input of the ALU	0: $B = \text{BusB}$ 1: $B = \text{Immediate}$
ExtOp	Determine logical or signed extension	0: logical extension 1: signed extension
ALUOP	Determine the operation for the ALU	0: AND 1: ADD 2: SUB
AdressSig	Determines the address for data stored in the memory	0: from register file 1: ALU result
DataInSig	Determines if the data stored in the memory from the registerfile or from ALU	0: data from register file 1: Immediate
MemRd	Enable read from memory	0: disable 1: enable
MemWr	Enable write to memory	0: disable 1: enable
Wbdata	Determine the return value from stage 5	0: data from ALU 1: data from memory
modeSig	control signal used to specify different modes of operation for(Branches)	0: BusA 1: R0
RegDst	Determines on which register to write	0: $RW = Rd$ 1: $RW = R7$

Table 2: Details about signals

### 2.1.2 Expressions for Control Bits(Rebal):

$$mode = LBs + BGTZ + BLTZ + BEQZ + BNEZ$$

$$ReqSrc2 = \sim(R\_Type)$$

$$RegWr1 = R - type + ADDI + ANDI + LW + Lbu + LBS$$

$$ReqWr2 = CALL$$

$$ALUSrc = R\_Type$$

$$ExtOP = BGT + BGTZ + BLT + BLTZ + BEQ + BEQZ + BNE + BNEZ + Lbu + Lbs$$

$$ALUOp = R_{Type} + ADDI + ANDI + LW + Lbu + LBS + sw$$

$$AdressSig = Sv$$

$$DataInSig = Sv$$

$$MemRd = LW + Lbu + LBS$$

$$MemWr = SW + Sv$$

$$Wbdata = LW + Lbu + LBS$$

$$modeSig = BGTZ + BLTZ + BEQZ + BNEZ$$

$$RegDst = CALL$$

### 2.1.3 Final Data path(Mohammad, Sondos, Rebal):

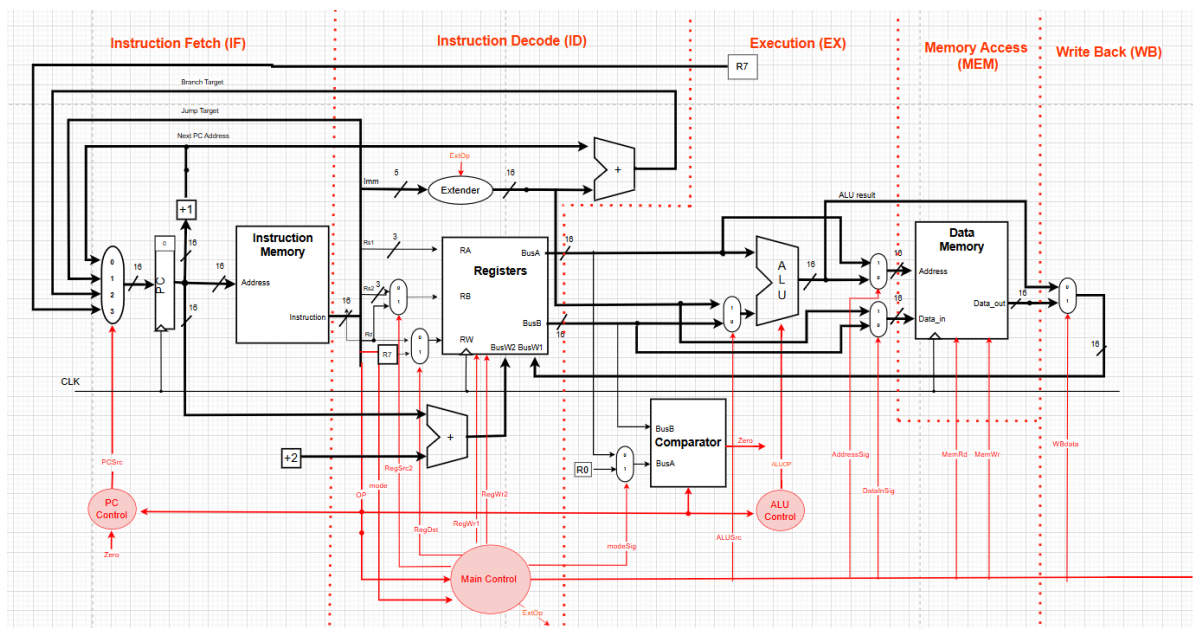


Figure 12: Final Data path

## 2.2 Modules:

### 2.2.1 Clock Generator (Mohammad):

 


Figure 13: Clock Generator\_tb

### 2.2.2 Instruction Fetch (Sondos):

 


Figure 14: Instruction Fetch\_tb

### 2.2.3 Data memory (Mohammad):

 


Figure 15: Data memory\_tb

### 2.2.4 ALU(Rebal):

 


Figure 16: ALU\_tb

## 2.2.5 Control Unit (Rebal):

 


Figure 17: Control Unit\_tb

## 2.2.6 Comparator(Sondos):

 


Figure 18: Comparator\_tb

## 2.2.7 PC (Mohammad):

 


Figure 19: PC\_tb

## 2.2.8 Register file (Sondos):

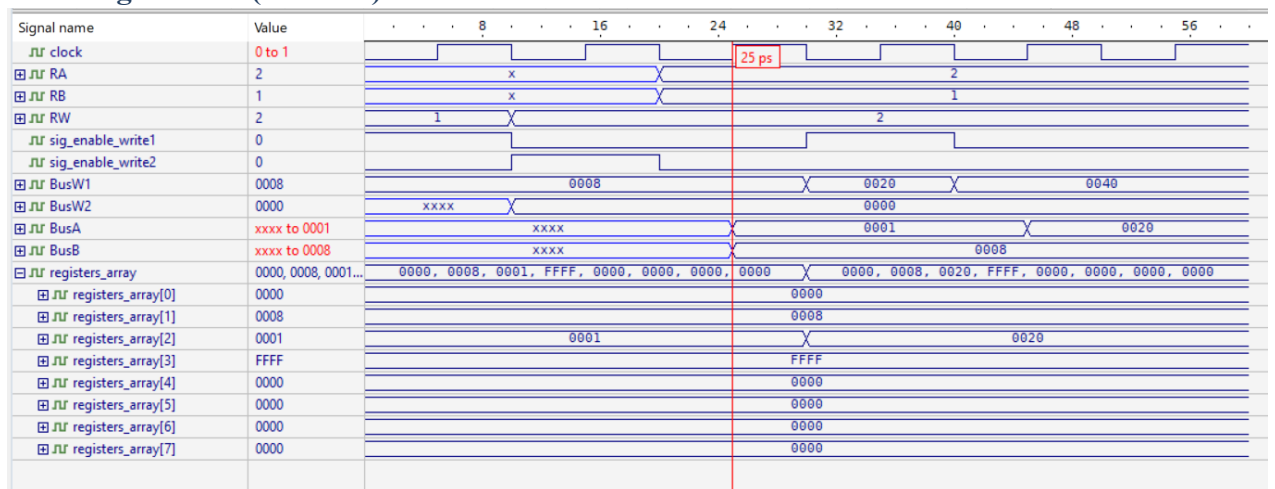


Figure 20: Register file\_tb

## 2.2.9 Constants (Rebal):

```

1 parameter
2 // Kept these just in case
3 // Levels
4
5 LOW = 1'b0,
6 HIGH = 1'b1,
7
8 // Instruction codes
9 // 4-bit instruction code
10
11 // R-Type Instructions
12
13 AND = 4'b0000, // Reg(Rd) = Reg(Rs1) & Reg(Rs2)
14 ADD = 4'b0001, // Reg(Rd) = Reg(Rs1) + Reg(Rs2)
15 SUB = 4'b0010, // Reg(Rd) = Reg(Rs1) - Reg(Rs2)
16
17 // I-Type Instructions
18
19 ADDI = 4'b0011, // Reg(Rd) = Reg(Rs1) + Immediate5
20 ANDI = 4'b0100, // Reg(Rd) = Reg(Rs1) + Immediate5
21 LW = 4'b0101, // Reg(Rd) = Mem(Reg(Rs1) + Imm_5)
22 LBU = 4'b0110, // Reg(Rd) = Mem(Reg(Rs1) + Imm_5)
23 LBS = 4'b0110, // Reg(Rd) = Mem(Reg(Rs1) + Imm_5)
24

```

Figure 21: Constants\_code

## 2.2.9 CPU (Sondos, Mohammad):

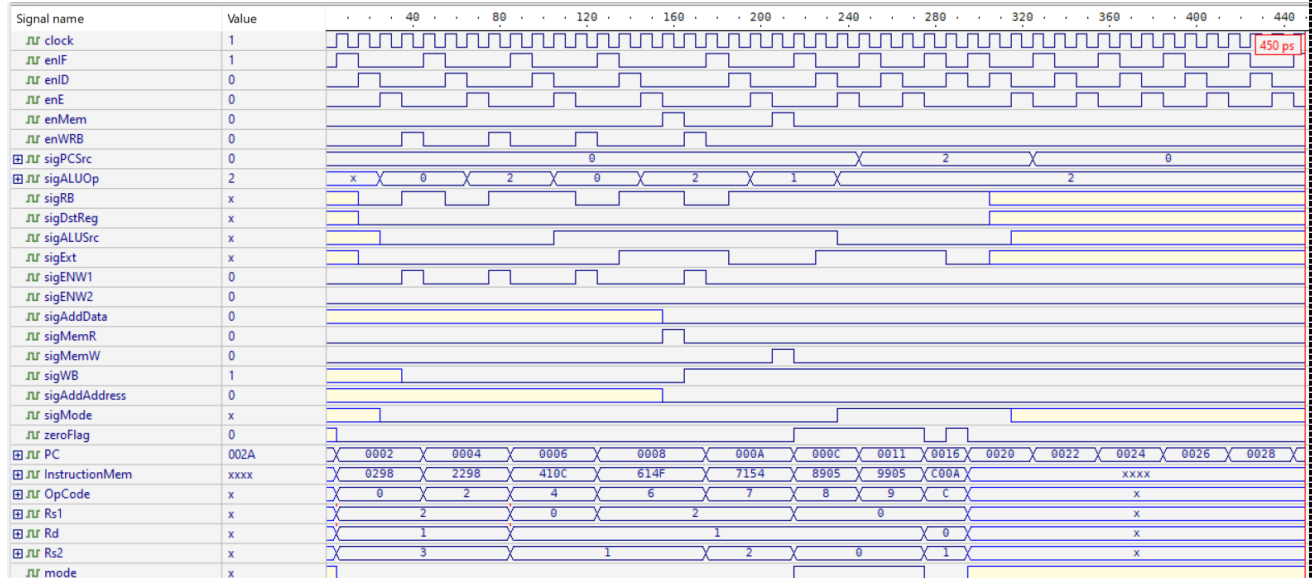


Figure 22: CPU\_tb



### **3. Conclusion:**

Designing a multi-cycle RISC processor involves a comprehensive understanding of computer architecture principles, including ISA, data path and control path design, control signal generation, and memory organization. Verification through simulation ensures the correctness and robustness of the processor. This project demonstrates the practical application of these theoretical concepts in developing a functional multi-cycle processor in Verilog.

## 4. Appendices:

### 4.1 The code for Constants:

parameter

// Kept these just in case

// Levels

LOW = 1'b0,

HIGH = 1'b1,

// Instruction codes

// 4-bit instruction code

// R-Type Instructions

AND = 4'b0000, //  $\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Reg(Rs2)}$

ADD = 4'b0001, //  $\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Reg(Rs2)}$

SUB = 4'b0010, //  $\text{Reg(Rd)} = \text{Reg(Rs1)} - \text{Reg(Rs2)}$

// I-Type Instructions

ADDI = 4'b0011, //  $\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Immediate5}$

ANDI = 4'b0100, //  $\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Immediate5}$

LW = 4'b0101, //  $\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm\_5})$

LBu = 4'b0110, //  $\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm\_5})$

LBs = 4'b0110, //  $\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm\_5})$

SW = 4'b0111, //  $\text{Mem}(\text{Reg(Rs1)} + \text{Imm\_14}) = \text{Reg(Rd)}$

BGT = 4'b1000, /\* if ( $\text{Reg(Rd)} > \text{Reg(Rs1)}$ )

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

BGTZ = 4'b1000, /\* if (Reg(Rd) > Reg(0))

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

BLT = 4'b1001, /\* if (Reg(Rd) < Reg(Rs1))

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

BLTZ = 4'b1001, /\* if (Reg(Rd) < Reg(R0))

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

BEQ = 4'b1010, /\* if (Reg(Rd) == Reg(Rs1))

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

BEQZ = 4'b1010, /\* if (Reg(Rd) == Reg(R0))

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

BNE = 4'b1011, /\* if (Reg(Rd) != Reg(Rs1))

Next PC = PC + sign\_extended (Imm) \*/

BNEZ = 4'b1011, /\* if (Reg(Rd) != Reg(Rs1))

Next PC = PC + sign\_extended (Imm)

else PC = PC + 2\*/

// J-Type Instructions

JMP = 4'b1100, // Next PC = {PC[15:10], Immediate}

CALL = 4'b1101, /\* Next PC = {PC[15:10], Immediate}

PC + 4 is saved on r15 \*/

RET = 4'b1110, // Next PC = r7

// S-Type Instructions

```

Sv = 4'b1111, // M[rs] = imm

// *Signals*

// PC src
// 2-bit select to determine next PC value

pcDefault = 2'b00, // PC = PC + 1
pcImm = 2'b01, // jump address
pcSgnImm = 2'b10, // branch target address
pcRET = 2'b11, // PC = R7(RET)

// Dst Reg
// 1-bit select to determine on which register to write

//R7 = 1'b0, // RW = R7
Rd = 1'b1, // RW = Rd

// RB
// 1-bit select to determine second register

Rs2 = 1'b0, // RB = Rs2
Rsd = 1'b1, // RB = Rd
//Rd = 1'b1, // RW = Rd

// En W
// 1-bit select to E/D write on registers

```

```

WD = 1'b0, // Write enabled
WE = 1'b1, // Write disabled

// ALU src
// 1-bit source select to determine first input of the ALU

Imm = 1'b0,    // B = Immediate
BusB = 1'b1, // B = BusB

// ALU op
// 2-bit select to determine operation of ALU

ALU_AND = 2'b00,
ALU_ADD = 2'b01,
ALU_SUB = 2'b10,

// Mem R
// 1-bit select to enable read from memory

MRD = 1'b0,    // Memory read disabled
MRE = 1'b1, // Memory read enabled

// Mem W
// 1-bit select to enable write to memory

MWD = 1'b0,    // Memory write disabled
MWE = 1'b1, // Memory write enabled

```

```

// WB
// 1-bit select to determine return value from stage 5

WBALU = 1'b0, // Data from ALU
WBMem = 1'b1, // Data from memory

// ext
// 1-bit select to determine logical or signed extension

logExt = 1'b0, // Logical extension
sgnExt = 1'b1, // Signed extension

//Data signal

// stack/mem
// 1-bit select to store address of data in memory or push on stack

//WBALU = 1'b0, // Data from ALU
BusA = 1'b1, // Calculate address of the memory

// address/data
// 1-bit select to determine source of data to be stored in memory

//Imm = 1'b0, // B = Immediate
//BusB = 1'b1, // B = BusB

// 8 registers

R0 = 3'd0, // zero register

```

```

R1 = 3'd1, // general purpose register
R2 = 3'd2, // general purpose register
R3 = 3'd3, // general purpose register
R4 = 3'd4, // general purpose register
R5 = 3'd5, // general purpose register
R6 = 3'd6, // general purpose register
R7 = 3'd7; // general purpose register

```

## 4.2 The code for comparator:

```

module comparator (
    input [15:0] BusA, // rs or R0
    input [15:0] BusB, // rd
    input [3:0] opCode, // operation code
    output reg zero // output: 1 if condition is true (branch taken), 0 otherwise
);

always @(*) begin
    case (opCode)
        4'b1000: zero = (BusB > BusA) ? 1 : 0; // BGT
        4'b1001: zero = (BusB > 16'd0) ? 1 : 0; // BGTZ
        4'b1010: zero = (BusB < BusA) ? 1 : 0; // BLT
        4'b1011: zero = (BusB < 16'd0) ? 1 : 0; // BLTZ
        4'b1100: zero = (BusB == BusA) ? 1 : 0; // BEQ
        4'b1101: zero = (BusB == 16'd0) ? 1 : 0; // BEQZ
        4'b1110: zero = (BusB != BusA) ? 1 : 0; // BNE
        4'b1111: zero = (BusB != 16'd0) ? 1 : 0; // BNEZ
        default: zero = 0; // Default case: no branch
    endcase
end

endmodule

```

### 4.3 The code for Control Unit:

```
`include "constants.v"
```

```
module controlUnit(
```

```
    clock,
```

```
    // signal outputs
```

```
    sigPCSrc,
```

```
    sigDstReg,
```

```
    sigRB,
```

```
    sigENW1,
```

```
    sigENW2,
```

```
    sigALUSrc,
```

```
    sigALUOp,
```

```
    sigExt,
```

```
    sigAddData,
```

```
    sigMemR,
```

```
    sigMemW,
```

```
    sigWB,
```

```
    sigAddAddress,
```

```
    sigMode,
```

```
    // Enable signals to be outputted by the CU
```

```
    enIF, // enable instruction fetch
```

```
    enID, // enable instruction decode
```

```
    enE, // enable execute
```

```
    enMem, // enable memory
```

```
    enWRB,
```



```

// inputs
zeroFlag,
mode,

// Opcode to determine signals
instructionCode
);

// ----- INPUTS -----

// clock
input wire clock;

// mode
input wire mode;

// zero flag and negative Flag
input wire zeroFlag;

// function code
input wire [3:0] instructionCode;

// ----- OUTPUTS -----

output reg [3:0] sigPCSrc = pcDefault;
output reg [1:0] sigALUOp;
output reg sigDstReg, sigRB, sigALUSrc, sigWB, sigExt, sigAddData, sigAddAddress, sigMode;

output reg sigENW1 = LOW,
        sigENW2 = LOW,

```

```

        sigMemW = LOW,
        sigMemR = LOW;

output reg enE = LOW,
        enIF = LOW,
        enID = LOW,
        enMem = LOW,
        enWRB = LOW;

// Code to determine stages and manage stage paths
`define STG_FTCH 3'b000
`define STG_DCDE 3'b001
`define STG_EXEC 3'b010
`define STG_MEM 3'b011
`define STG_WRB 3'b100
`define STG_INIT 3'b101

reg [2:0] currentStage = `STG_INIT;
reg [2:0] nextStage = `STG_FTCH;

always@(posedge clock) begin

    currentStage = nextStage;

end

always@(posedge clock) begin

    case (currentStage)

```

```

`STG_INIT: begin
    enIF = LOW;
    nextStage <= `STG_FTCH;
end

`STG_FTCH: begin
    // Disable all previous stages leading up to IF
    enID = LOW;
    enE = LOW;
        enMem = LOW;
        enWRB = LOW;

    // Disable signals
    sigENW1 = LOW;
        sigENW2 = LOW;
    sigMemW = LOW;
    sigMemR = LOW;

    // Enable IF
    enIF = HIGH; // Fetch after finding PC src

    // Determine next stage
    nextStage <= `STG_DCDE;

    // Determine next PC through testing of opcodes
    if (instructionCode == BGT && zeroFlag || instructionCode == BLT && zeroFlag ||
instructionCode == BEQ && zeroFlag || instructionCode == BNE && zeroFlag || instructionCode ==
BNEZ && zeroFlag || BGTZ && zeroFlag || BLTZ && zeroFlag ) begin

        sigPCSrc = pcSgnImm;

```

```

end else if (instructionCode == JMP || instructionCode == CALL) begin

    sigPCSrc = pcImm;

end else if (instructionCode == RET) begin

    sigPCSrc = pcRET;          //R7

end else begin

    sigPCSrc = pcDefault;

end

end

end

`STG_DCDE: begin
    // Disable all previous stages leading up to ID
    enIF = LOW;

    // Enable IF
    enID = HIGH;

    // Next stage is determined by opcode
    if (instructionCode == CALL || instructionCode == RET || instructionCode
== JMP) begin
        nextStage <= `STG_FTCH;
    end

```

```

else begin
    nextStage <= `STG_EXEC;
end

sigRB=(instructionCode == AND || instructionCode == ADD ||
instructionCode == SUB) ? LOW : HIGH;
sigENW1= LOW;
sigENW2 =LOW;

sigExt=(instructionCode==BNEZ||instructionCode==BNE||instructionCode==BEQZ||instructionCo
de==BEQ||instructionCode==BLTZ||instructionCode==BLT||instructionCode==BGTZ||instructionCode
==BGT||instructionCode==LBs||instructionCode==LBu) ? HIGH : LOW;

sigDstReg =(instructionCode == CALL)? HIGH : LOW;

end

`STG_EXEC: begin

    // Disable all previous stages leading up to execute stage
    enID = LOW;

    //sigENW1 = !sigENW1;

    // Enable execute stage
    enE = HIGH;

    sigALUSrc=(instructionCode == ADDI || instructionCode == ANDI ||
instructionCode == LW|| instructionCode == LBu || instructionCode == LBs|| instructionCode == SW)?
HIGH : LOW;

    sigMode=(instructionCode==BGTZ &&
mode==1||instructionCode==BLTZ && mode==1||instructionCode==BEQZ &&

```

```
mode==1||instructionCode==BNEZ && mode==1 ||instructionCode==LBs && mode==1) ? HIGH :  
LOW;
```

```
// Next stage is determined by opcode
```

```
if (instructionCode == LW || instructionCode == LBU || instructionCode == SW ||  
instructionCode == LBs || instructionCode == Sv ) begin
```

```
    nextStage <= `STG_MEM;
```

```
end else if (instructionCode == AND || instructionCode == ADD || instructionCode == SUB ||  
instructionCode == ANDI || instructionCode == ADDI) begin
```

```
    nextStage <= `STG_WRB;
```

```
end else begin
```

```
    nextStage <= `STG_FTCH;
```

```
end
```

```
// Set ALUOp signal based on the opcodes
```

```
if (instructionCode == AND || instructionCode == ANDI) begin
```

```
    sigALUOp = ALU_AND;
```

```
end else if (instructionCode == ADD || instructionCode == ADDI || instructionCode == LW ||  
instructionCode == SW) begin
```

```
    sigALUOp = ALU_ADD;
```

```

end else begin

    sigALUOp = ALU_SUB;

end

    sigENW1 = LOW;

sigENW2 = LOW;
end

`STG_MEM: begin
    enMem = HIGH;

    // Disable all previous stages leading up to memory stage
    enE = LOW;
    enID = LOW;

    // Enable memory stage

    // Next stage determined by opcodes
    nextStage <= (instructionCode == LW || instructionCode == LBu || instructionCode == LBs) ?
`STG_WRB : `STG_FTCH;

    // Memory write is determined by the SW instruction
    sigMemW      =(instructionCode==Sv||instructionCode==SW)? HIGH :
LOW;

    // Memory Read is determined by Load instructions
    sigMemR=(instructionCode==LBs||instructionCode==LBu||instructionCode==LW) ? HIGH
: LOW;

    // Signals determined by opcodes

```

```
sigAddData=(instructionCode==Sv)? HIGH : LOW;
```

```
sigAddAddress=(instructionCode==Sv)? HIGH : LOW;
```

```
sigExt=(instructionCode==BNEZ||instructionCode==BNE||instructionCode==BEQZ||instructionCode==BEQ||instructionCode==BLTZ||instructionCode==BLT||instructionCode==BGTZ||instructionCode==BGT||instructionCode==LBs||instructionCode==LBu) ? HIGH : LOW;
```

```
end
```

```
`STG_WRB: begin
```

```
    enWRB=HIGH;
```

```
    // Disable all previous stages leading up to WRB
```

```
    sigMemW = LOW;
```

```
    sigMemR = LOW;
```

```
    enE = LOW;
```

```
    enMem = LOW;
```

```
    // Enable WRB stage
```

```
    sigRB =~(instructionCode == AND || instructionCode == ADD ||  
instructionCode == SUB) ?LOW : HIGH;
```

```
    // Next stage following WRB is IF
```

```
    nextStage <= `STG_FTCH;
```

```
    // Enable writing to register filw
```

```
    sigENW1=(instructionCode == AND || instructionCode == ADD ||  
instructionCode ==  
SUB||instructionCode==LBs||instructionCode==LBu||instructionCode==LW||instructionCode==ADDI||i  
nstructionCode==ANDI)? HIGH : LOW;
```



```

        sigENW2=(instructionCode ==CALL)? HIGH : LOW;

        // Determine the register to write to

        sigWB
        =(instructionCode==LBs||instructionCode==LBU||instructionCode==LW) ? HIGH : LOW;

        // Set to 1 for all instructions

        sigDstReg =(instructionCode == CALL)? HIGH : LOW;


        sigExt=(instructionCode==BNEZ||instructionCode==BNE||instructionCode==BEQZ||instructionCo
de==BEQ||instructionCode==BLTZ||instructionCode==BLT||instructionCode==BGTZ||instructionCode
==BGT||instructionCode==LBs||instructionCode==LBU) ? HIGH : LOW;


        end

    endcase

end

endmodule

```

#### 4.4 The code for alu:

```

`include "constants.v"

module ALU(A, B, Output, ALUop,EN);

    // ----- SIGNALS & INPUTS -----

    // chip select for ALU operation
    input wire [3:0] ALUop;

    //Enable flag

```

```

input wire EN;

// operands
input wire [15:0] A, B;

// ----- OUTPUTS -----

output reg      [15:0] Output;

// ----- LOGIC -----

always @(EN) begin
    // #1 // To wait for ALU source mux to select operands
    case (ALUop)
        AND: Output <= A & B;
        ANDI: Output <= A & B;
        ADD: Output <= A + B;
        ADDI: Output <= A + B;
        LW: Output <= A + B;
        LBU: Output <= A + B;
        LBS: Output <= A + B;
        SW: Output <= A + B;
        SUB: Output <= A - B;
        default: Output <= 0;
    endcase
end

initial begin

```

```

        if (EN == LOW)begin
            Output = 16'd0;
        end
    end
end

```

```
endmodule
```

#### 4.5 The code for ClockGenerator:

// generates clock square wave with 10ns period

```

module ClockGenerator (
    clock
);

initial begin
    $display("(%0t) > initializing clock generator ...", $time);
end

output reg clock=0; // starting LOW is important for first instruction fetch

always #5 begin
    clock=~clock;
end

endmodule

```

#### 4.6 The code for data Memory:

// data memory with 256 cells of 16 bits each

```

module dataMemory(clock, AddressBus, InputBus, OutputBus, sig_enable_write,
sig_enable_read,memory);

```

```

    // ----- SIGNALS -----

```

```

// clock
input wire clock;

// enable write signal
input wire sig_enable_write;

// enable write signal
input wire sig_enable_read;

// ----- INPUTS -----

// address bus
input wire [15:0] AddressBus;

// MBR - in
input wire [15:0] InputBus;

// ----- OUTPUTS -----

// MBR - out
output reg [15:0] OutputBus;

// ----- INTERNALS -----

// memory
output reg [15:0] memory [0:255];

// ----- LOGIC -----

```

```

// read instruction at positive edge of clock
always @(posedge clock) begin
    if (sig_enable_read) begin
        OutputBus <= memory[AddressBus];
    end else if (sig_enable_write) begin
        memory[AddressBus] <= InputBus;
    end
end

// ----- INITIALIZATION -----

initial begin

    // store some initial data
    memory[0] = 16'd10;
    memory[1] = 16'd5;
    memory[16] = 16'd9;

end

endmodule

```

#### 4.7 The code for instruction Memory:

```

module instructionMemory(clock, AddressBus, InstructionReg);

```

```

// ----- INPUTS -----

```

```

// clock

```

```

input wire clock;

```

```

// address bus
input wire [15:0] AddressBus;

// ----- OUTPUTS -----

// instruction register
output reg [15:0] InstructionReg;

// ----- INTERNALS -----

// instruction memory
reg [15:0] instruction_memory [0:255]; // Each instruction is 16 bits, memory size can be adjusted as
needed

// ----- LOGIC -----

always @(posedge clock) begin
    InstructionReg <= instruction_memory[AddressBus];
end

// ----- INITIALIZATION -----

initial begin

    // instruction formats:
    // R-Type Instruction Format
    // Opcode_4, Rd_3, Rs1_3, Rs2_3, Unused_3

    // I-Type Instruction Format

```

```

// Opcode_4, m_1, Rd_3, Rs1_3, Immediate_5

// J-Type Instruction Format
// Opcode_4, Jump_Offset_12

// S-Type Instruction Format
// Opcode_4, Rs_3, Immediate_9
    /*****/

// R-Type Instructions
// AND R1, R2, R3
instruction_memory[0] = {4'b0000, 3'b001, 3'b010, 3'b011, 3'b000}; // AND R1, R2, R3
// ADD R1, R2, R3
instruction_memory[1] = {4'b0001, 3'b001, 3'b010, 3'b011, 3'b000}; // ADD R1, R2, R3
// SUB R1, R2, R3
instruction_memory[2] = {4'b0010, 3'b001, 3'b010, 3'b011, 3'b000}; // SUB R1, R2, R3

// I-Type Instructions
// ADDI R1, R0, 8
instruction_memory[3] = {4'b0011, 1'b0, 3'b001, 3'b000, 5'd8}; // ADDI R1, R0, 8
// ANDI R1, R0, 12
instruction_memory[4] = {4'b0100, 1'b0, 3'b001, 3'b000, 5'd12}; // ANDI R1, R0, 12
// LW R1, 10(R2)
instruction_memory[5] = {4'b0101, 1'b0, 3'b001, 3'b010, 5'd10}; // LW R1, 10(R2)
// LBU R1, 15(R2)
instruction_memory[6] = {4'b0110, 1'b0, 3'b001, 3'b010, 5'd15}; // LBU R1, 15(R2)
// LBS R1, 15(R2)
instruction_memory[7] = {4'b0110, 1'b1, 3'b001, 3'b010, 5'd15}; // LBS R1, 15(R2)
// SW R1, 20(R2)
instruction_memory[8] = {4'b0111, 1'b0, 3'b001, 3'b010, 5'd20}; // SW R1, 20(R2)

```

```

// BGT R1, R2, 5
instruction_memory[9] = {4'b1000, 1'b0, 3'b001, 3'b010, 5'd5}; // BGT R1, R2, 5
// BGTZ R1, 5
instruction_memory[10] = {4'b1000, 1'b1, 3'b001, 3'b000, 5'd5}; // BGTZ R1, 5
// BLT R1, R2, 5
instruction_memory[11] = {4'b1001, 1'b0, 3'b001, 3'b010, 5'd5}; // BLT R1, R2, 5
// BLTZ R1, 5
instruction_memory[12] = {4'b1001, 1'b1, 3'b001, 3'b000, 5'd5}; // BLTZ R1, 5
// BEQ R1, R2, 5
instruction_memory[13] = {4'b1010, 1'b0, 3'b001, 3'b010, 5'd5}; // BEQ R1, R2, 5
// BEQZ R1, 5
instruction_memory[14] = {4'b1010, 1'b1, 3'b001, 3'b000, 5'd5}; // BEQZ R1, 5
// BNE R1, R2, 5
instruction_memory[15] = {4'b1011, 1'b0, 3'b001, 3'b010, 5'd5}; // BNE R1, R2, 5
// BNEZ R1, 5
instruction_memory[16] = {4'b1011, 1'b1, 3'b001, 3'b000, 5'd5}; // BNEZ R1, 5

// J-Type Instructions
// JMP 10
instruction_memory[17] = {4'b1100, 12'd10}; // JMP 10
// CALL 20
instruction_memory[18] = {4'b1101, 12'd20}; // CALL 20
// RET
instruction_memory[19] = {4'b1110, 12'b0}; // RET

// S-Type Instructions
// Sv R2, 255
instruction_memory[20] = {4'b1111, 3'b010, 9'd255}; // Sv R2, 255
end

```



```
endmodule
```

#### 4.8 The code for register File:

```
module registerFile(clock, RA, RB, RW, sig_enable_write1,sig_enable_write2, BusW1, BusW2,  
BusA, BusB,registers_array);
```

```
    input wire clock;
```

```
    input wire sig_enable_write1 , sig_enable_write2;
```

```
    input wire [2:0] RA, RB, RW;
```

```
    output reg [15:0] BusA, BusB;
```

```
    input wire [15:0] BusW1,BusW2;
```

```
    output reg [15:0] registers_array [0:7];
```

```
    always @(posedge clock) begin
```

```
        if(sig_enable_write1==0 && sig_enable_write2==0) begin
```

```
            BusB = registers_array[RB];
```

```
            BusA = registers_array[RA];
```

```
        end
```

```
    end
```

```
    always @(posedge (sig_enable_write1 || sig_enable_write2) ) begin
```

```
        if ( RW != 3'b0 && sig_enable_write1) begin
```

```

        registers_array[RW] = BusW1;
    end
    if ( RW != 3'b0 && sig_enable_write2) begin
        registers_array[RW] = BusW2;
    end

end

initial begin
    // Initialize registers to be zeros
    registers_array[0] <= 16'h0000;
    registers_array[1] <= 16'h4444;
    registers_array[2] <= 16'h0001;
    registers_array[3] <= 16'hFFFF;
    registers_array[4] <= 16'h0000;
    registers_array[5] <= 16'h0000;
    registers_array[6] <= 16'h0000;
    registers_array[7] <= 16'h0000;

end

endmodule

```

#### 4.9 The code for riscProcessor:

```

`include "constants.v"

module riscProcessor();

    initial begin
        #0
        $display("(%0t) > initializing processor ...", $time);

        #450 $finish;
    end
endmodule

```

```

end

// clock generator wires/registers
wire clock;
wire enIF, enID, enE, enMem, enWRB;

// ----- Control Unit -----

wire [3:0] sigPCSrc;
wire [1:0] sigALUOp;
wire sigRB, sigDstReg, sigALUSrc, sigExt, sigENW1, sigENW2, sigAddData, sigMemR,
sigMemW, sigWB, sigAddAddress, sigMode;
wire zeroFlag;

// ----- Instruction Memory -----

// instruction memory wires/registers
wire [15:0] PC; // output of PC Module input to instruction memory
reg [15:0] InstructionMem; // output if instruction memory, input to other modules

// Instruction Parts
wire [3:0] OpCode; // function code

// R-Type
wire [2:0] Rs1, Rd, Rs2; // register selection
wire mode;

```

```

// ----- Register File -----

wire [2:0] RA, RB, RW;
wire [15:0] BusA, BusB, BusW1 , BusW2,BusAC;


// ----- ALU -----

wire [15:0] A, B;
wire [15:0] ALURes;


// ----- Data Memory -----

wire [15:0]    AddressBus, InputBus,OutputBus;
assign AddressBus = (sigAddAddress == LOW) ? ALURes : BusA;
assign InputBus = (sigAddData == LOW ) ? BusB : extendedImm5;


// ----- Assignment -----


// Function Code
assign OpCode = InstructionMem[15:12];


// R-Type

assign Rd = (OpCode==ADD ||OpCode== AND ||OpCode==SUB
||OpCode==Sv)?InstructionMem[11:9] :InstructionMem[10:8] ;
assign Rs1 = (OpCode==ADD ||OpCode== AND ||OpCode==SUB ||OpCode==Sv)?
InstructionMem[8:6] : InstructionMem[7:5];
assign Rs2 = InstructionMem[5:3];


// I-Type

wire signed [4:0] Imm5;
assign Imm5 = InstructionMem[4:0];
assign mode = InstructionMem[11];

```

```

// J-Type
wire [11:0] Imm12;
assign Imm12 = InstructionMem[11:0];

// S-Type
wire [8:0] Imm9;
assign Imm9 = InstructionMem[8:0];

// ----- Register File -----
wire [15:0] WBOutput;
wire EnReg;
assign RA = Rs1;
assign RB = (sigRB == LOW) ? Rs2 : Rd;
assign RW = (sigDstReg == LOW) ? Rd : 3'b111;
assign EnReg = (enID || enWRB);
assign BusW1 = WBOutput;
assign BusW2 = (PC + 2'd2);

// ----- ALU -----
wire [15:0] extendedImm5 ,extendedImm12 ;
wire [15:0] signExtendedImm, zeroExtendedImm;
assign signExtendedImm = {{11{Imm5[4]}}, Imm5};
assign zeroExtendedImm = {{11{1'b0}}, Imm5};
assign extendedImm5 = (sigExt == HIGH) ? signExtendedImm: zeroExtendedImm;
assign A = BusA;
assign B = (sigALUSrc == LOW) ? BusB : extendedImm5;

```

```
assign BusAC = (sigMode==LOW) ? BusA : 3'b000;
assign extendedImm12 = {{4{Imm12[11]}}, Imm12};
```

```
ClockGenerator clock_generator(.clock(clock) );
```

```
// -----
// ----- Control Unit -----
// -----
```

```
controlUnit cu(
```

```
    clock,
```

```
    // signal outputs
```

```
    sigPCSrc,
```

```
    sigDstReg,
```

```
    sigRB,
```

```
    sigENW1,
```

```
    sigENW2,
```

```
    sigALUSrc,
```

```
    sigALUOp,
```

```
    sigExt,
```

```
    sigAddData,
```

```
    sigMemR,
```

```
    sigMemW,
```

```
    sigWB,
```

```
    sigAddAddress,
```

```
    sigMode,
```

```
    // Enable signals to be outputted by the CU
```

```

    enIF, // enable instruction fetch
    enID, // enable instruction decode
    enE, // enable execute
    enMem, // enable memory
    enWRB,

    // inputs
    zeroFlag,
    mode,

    // Opcode to determine signals
    OpCode
);

// -----
// ----- PC Module -----
// -----

pcModule pcMod(enIF, PC, extendedImm5, extendedImm12, r7, sigPCSrc);

// -----
// ----- Instruction Memory -----
// -----

instructionMemory insMem(enIF, PC, InstructionMem);

// -----
// ----- Register File -----
// -----

```

```

wire [15:0] registers_array [0:7];
wire [15:0] r7 = registers_array[7];

registerFile regFile(clock, RA, RB, RW, sigENW1,sigENW2, BusW1, BusW2, BusA,
BusB,registers_array);

// -----
// ----- ALU -----
// -----

ALU alu(A, B, ALURes, OpCode, enE);

// -----
// ----- Comparator -----
// -----

comparator comp(BusAC,BusB,OpCode,zeroFlag);

// -----
// ----- Data Memory -----
// -----

wire [15:0] memory [0:255];
dataMemory dataMem(enMem, AddressBus, InputBus, OutputBus, sigMemW, sigMemR,memory);

// -----
// ----- Write Back -----
// -----

assign WBOutput = (sigWB == 0) ? ALURes : OutputBus;

endmodule

```